

Design & Simulate 7 Ex2.1

ECE2204 CRN:82929


Jacob Abel

September 13, 2018

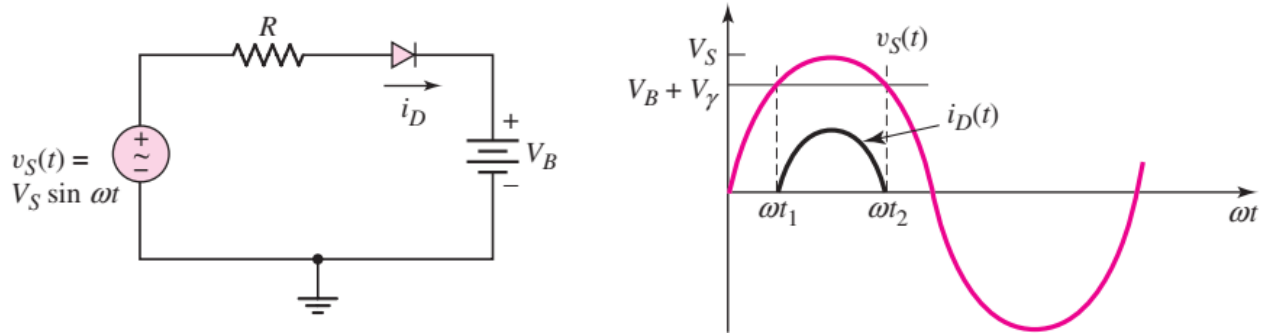Problem 7.2-1.a.1:

Design

Determine the currents and voltages in a half-wave rectifier circuit. Consider the circuit shown below. Assume $V_B = 5V$, $R = 200\Omega$, $V_\gamma = 0.73V$, and, $v_S(t) = 12 \sin \omega t$. Determine the peak diode current, maximum reverse-bias diode voltage, and the fraction of the cycle over which the diode is conducting.



$$i_D(\text{peak}) = \frac{V_S - V_B - V_\gamma}{R} = \frac{12V - 5V - 0.73V}{200\Omega} = 31.35mA \quad (1)$$

$$i_D = i_D(\text{peak}) \sin \omega t = 31.35mA \sin \omega t \quad (2)$$

$$v_R(\text{max}) = V_S + V_B = 12V + 5V = 17V \quad (3)$$

$$\omega t_1 = v_S^{-1}(V_B + V_\gamma) = \arcsin\left(\frac{V_B + V_\gamma}{v_S}\right) = \arcsin\left(\frac{5V + 0.73V}{12}\right) = 28.52^\circ \quad (4)$$


$$\omega t_2 = v_S^{-1}(V_B + V_\gamma) = \text{supplement}(\omega t_1) = 180^\circ - \omega t_1 = 180^\circ - 28.52^\circ = 151.48^\circ \quad (5)$$

$$\%t = \frac{\omega t_2 - \omega t_1}{360^\circ} = \frac{151.48^\circ - 28.52^\circ}{360^\circ} = 0.341\bar{5} = 34.16\% \quad (6)$$

The peak diode current is $i_D(\text{peak}) = 31.35mA$. The maximum reverse-bias diode voltage is $v_R = 17V$, and the fraction of each cycle that the diode is conducting is $\%t = 34.16\%$

Validation

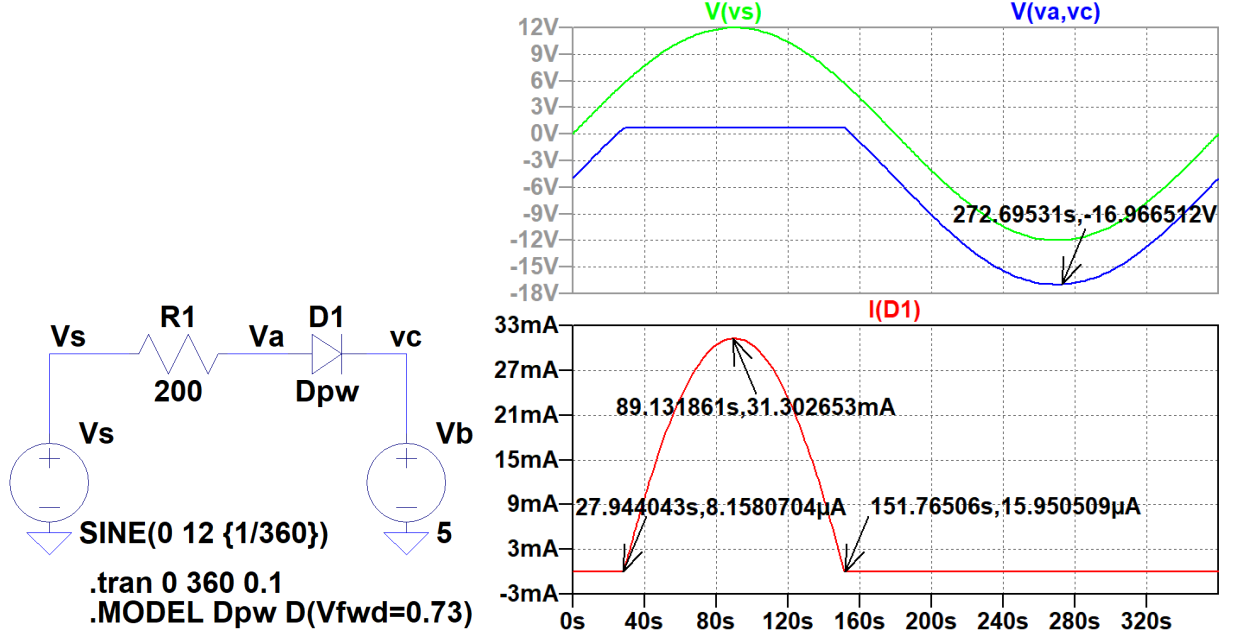LTSpice Implementation (accurate with < 1% deviation from design result)



$$Err_{V_R} = \frac{|17 - 16.966|}{17} = 0.002 = 0.2\%$$

$$Err_{i_D(\text{peak})} = \frac{|31.35 - 31.30|}{31.35} = 0.0015 = 0.15\%$$

$$Err_{\%t} = \frac{|0.3416 - \frac{151.7 - 27.9}{360}|}{34.16} = 0.000007 = 0.00\%$$

$$Err_{Avg} = \frac{0.20 + 0.15 + 0.00}{3} = 0.12\%$$


Problem 7.2-1.b.1:

The problem is derived from problem 2.3 on page 112 of the textbook by changing the values, making R dependent, and fixing the peak diode current.

Design

A half-wave rectifier such as shown below has a peak diode current of $I_D = 2mA$. The input is $V_I = 120V_{rms}$, $f = 60Hz$ signal and the transformer is a 10 : 1 step down transformer. The diode has a cut-in voltage of $V_\gamma = 1.2V$. Assume $r_f = 0$.

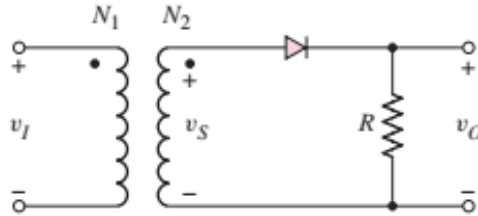Determine the value of the resistor R , the peak output voltage, the fraction (percent) of a cycle that $v_O > 0$, the average output voltage, and the average current in the load.



$$\omega = 120\pi \quad (7)$$

$$v_I = 120V_{rms} = 120\sqrt{2}V \sin(\omega t) \quad (8)$$

$$v_S = \frac{1}{10} 120\sqrt{2}V \sin(\omega t) = 12\sqrt{2}V \sin(120\pi t) \quad (9)$$

$$I_D = \frac{v_S - v_\gamma}{R} \quad (10)$$

$$\Rightarrow R = \frac{v_S - v_\gamma}{I_D} = \frac{12\sqrt{2} - 1.2V}{2mA} = 7885\Omega \quad (11)$$

$$\omega t_1 = v_S^{-1}(V_\gamma) = \arcsin\left(\frac{V_\gamma}{v_S}\right) = \arcsin\left(\frac{1.2V}{12\sqrt{2}V}\right) = 4.055^\circ \quad (12)$$

$$\omega t_2 = v_S^{-1}(V_\gamma) = \text{supplement}(\omega t_1) = 180^\circ - \omega t_1 = 180^\circ - 4.055^\circ = 175.945^\circ \quad (13)$$

$$\%t = \frac{\omega t_2 - \omega t_1}{360^\circ} = \frac{175.945^\circ - 4.055^\circ}{360^\circ} = 0.47747\bar{2} = 47.75\% \quad (14)$$

$$V_O = V_S - V_\gamma = 12\sqrt{2}V - 1.2V = 15.77V \quad (15)$$

$$v_O = V_O \sin(\omega t) = 15.77V \sin(\omega t) \quad (16)$$

$$v_{O\text{avg}} = \frac{V_O}{\omega} \int_{\omega t_1}^{\omega t_2} \sin(\omega t) d\omega t = \frac{15.77V}{2\pi} \int_{4.055^\circ}^{175.945^\circ} \sin(\omega t) d\omega t = 5.0075V \quad (17)$$


$$i_L = i_D = 2mA \sin(120\pi t) \quad (18)$$

$$i_{L\text{avg}} = \frac{I_L}{\omega} \int_{\omega t_1}^{\omega t_2} \sin(\omega t) d\omega t = \frac{2mA}{2\pi} \int_{4.055^\circ}^{175.945^\circ} \sin(\omega t) d\omega t = 635.1\mu A \quad (19)$$

The the value of the resistor is $R = 7885\Omega$, the peak output voltage is $V_O = 15.77V$, the fraction (percent) of a cycle that $v_O > 0$ is $\%t = 47.75$, the average output voltage is $V_{O\text{avg}} = 5.0075V$, and the average current in the load is $I_{L\text{avg}} = 635.1\mu A$.

Validation

LTSpice Implementation

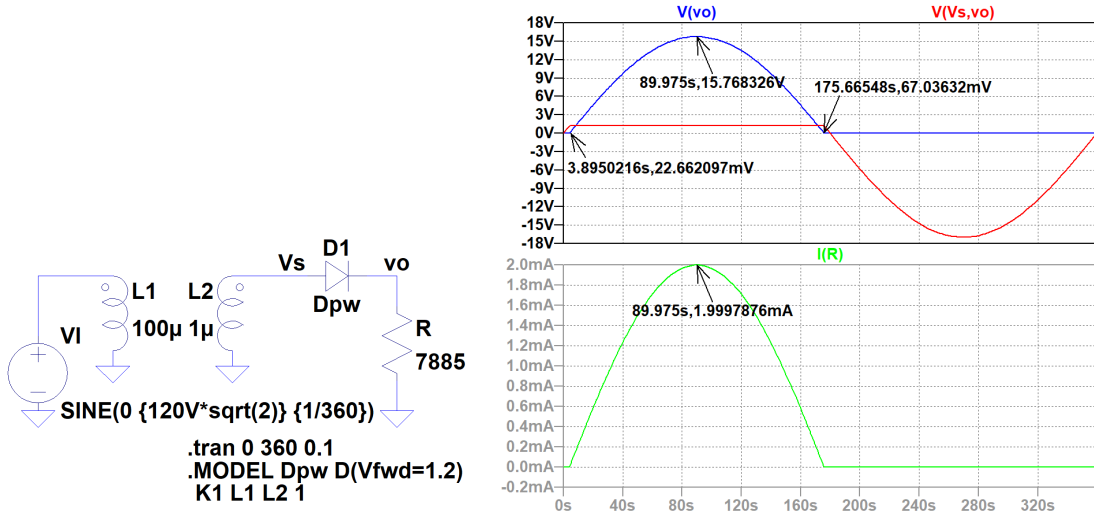

$$Err_{V_O} = \frac{|15.77 - 15.768|}{15.77} = 0.01\%$$

$$Err_{I_{Lavg}} = \frac{|635.1 - 610.91|}{635.1} = 3.80\%$$

$$Err_{Avg} = \frac{0.01 + 3.80 + 3.80 + 0.08}{4} = 1.92\%$$

$$Err_{V_{Oavg}} = \frac{|5.0075 - 4.817|}{5.0075} = 3.80\%$$

$$Err_{\%t} = \frac{|0.4775 - \frac{175.665 - 3.895}{360}|}{0.4775} = 0.08\%$$

Error above 1% is due to measurement error.

This assignment should demonstrate a basic understanding of manipulating basic half wave diode rectification circuits.

I have neither given nor received unauthorized assistance on this assignment.