


Homework 3

ECE2504 CRN:82729

Jacob Abel

September 17, 2017

Question 1: (6 pts)

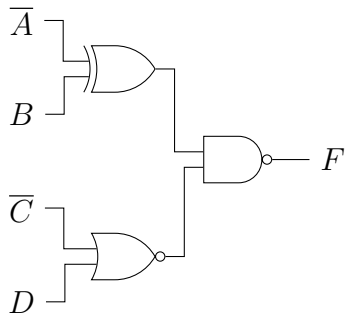

a) Write the logic equation for the variable F in the circuit below, as implemented.

$$F = (\overline{A} \oplus B)(\overline{\overline{C} + D})$$

b) Complete the truth table.

| A | B | C | D | $\overline{A} \oplus B$ | $\overline{\overline{A} + B}$ | F |
|---|---|---|---|-------------------------|-------------------------------|---|
| 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 |

| A | B | $\overline{A} \oplus B$ |
|---|---|-------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| A | B | $\overline{A} \oplus B$ |
|---|---|-------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| A | B | $\overline{\overline{A} + B}$ |
|---|---|-------------------------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

- c) Find an equivalent expression in sum-of-products form. (Hint: you can check your result by verifying that the truth table remains the same.)

$$F(A, B, C, D) = \Sigma m(0, 1, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 15)$$

$$\begin{aligned} F(A, B, C, D) = & \bar{A} \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} \bar{B} C \bar{D} + \bar{A} \bar{B} C D + \bar{A} B \bar{C} \bar{D} + \bar{A} B \bar{C} D \\ & + \bar{A} B C \bar{D} + \bar{A} B C D + A \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} D + A \bar{B} C \bar{D} + A \bar{B} C D \\ & + A B \bar{C} \bar{D} + A B \bar{C} D + A B C \bar{D} \end{aligned}$$

$$\begin{aligned} F(A, B, C, D) = & \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} D + A \bar{B} \bar{C} D + \bar{A} \bar{B} C \bar{D} + A \bar{B} C \bar{D} \\ & + \bar{A} B \bar{C} \bar{D} + A B \bar{C} \bar{D} + \bar{A} B \bar{C} D + A B \bar{C} D + \bar{A} B C \bar{D} \\ & + A B C \bar{D} + A \bar{B} C \bar{D} + \bar{A} B C \bar{D} \end{aligned}$$

$$\begin{aligned} F(A, B, C, D) = & (\bar{A} + A)(\bar{B} \bar{C} \bar{D} + \bar{B} \bar{C} D + \bar{B} C \bar{D} + B \bar{C} \bar{D} + B \bar{C} D + B C \bar{D}) \\ & + A \bar{B} C \bar{D} + \bar{A} B C \bar{D} \end{aligned}$$

$$\begin{aligned} F(A, B, C, D) = & \bar{B} \bar{C} \bar{D} + B \bar{C} \bar{D} + \bar{B} \bar{C} D + B \bar{C} D + \bar{B} C \bar{D} + B C \bar{D} \\ & + A \bar{B} C \bar{D} + \bar{A} B C \bar{D} \end{aligned}$$


$$F(A, B, C, D) = (\bar{B} + B)(\bar{C} \bar{D} + \bar{C} D + C \bar{D}) + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

$$F(A, B, C, D) = \bar{C} \bar{D} + C \bar{D} + \bar{C} D + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

$$F(A, B, C, D) = (\bar{C} + C)(\bar{D} + D) + \bar{C} \bar{D} + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

$$F(A, B, C, D) = D + \bar{C} \bar{D} + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

Question 2: (6 pts)

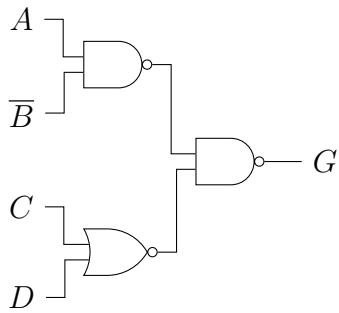

- a) Write the logic equation for the variable F in the circuit below, as implemented.

$$G = \overline{(\overline{A\overline{B}})} \overline{(C + D)}$$

- b) Complete the truth table.

| A | B | C | D | $\overline{(\overline{A\overline{B}})}$ | $\overline{(C + D)}$ | G |
|---|---|---|---|---|----------------------|---|
| 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 |

| A | B | $\overline{(\overline{A\overline{B}})}$ |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| A | B | $\overline{A\overline{B}}$ |
|---|---|----------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| A | B | $\overline{(A + B)}$ |
|---|---|----------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

- c) Find an equivalent expression in product-of-sums form. (Hint: you can check your result by verifying that the truth table remains the same.)

$$G(A, B, C, D) = \Pi m(0, 4, 12)$$

$$G(A, B, C, D) = (A + B + C + D)(A + \overline{B} + C + D)(\overline{A} + \overline{B} + C + D)$$

$$G(A, B, C, D) = (AB' + AC + AD + BA' + BC + C + CD + D)(A + \overline{B} + C + D)$$

$$G(A, B, C, D) = (AB' + AC + AD + ACD + B'D + A'BC + C + CD + A'BD + D)$$

Question 3: (3 pts) Use Boolean algebra to prove that $wxy' + xy'z' + xy + y'z = x + y'z$

$$wx\bar{y} + x\bar{y}\bar{z} + xy + \bar{y}z = x + \bar{y}z$$

$$x\bar{y}(w + \bar{z}) + xy + \bar{y}z = x + \bar{y}z$$

$$(\bar{y} + y)(x(w + \bar{z}) + 1) + \bar{y}z = x + \bar{y}z$$


$$x + \bar{y}z = x + \bar{y}z$$

Question 4: (10 pts) Given the Boolean function $F = x'y'z' + x'yz' + xy'z + xyz$

a) List the truth table.

| x | y | z | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

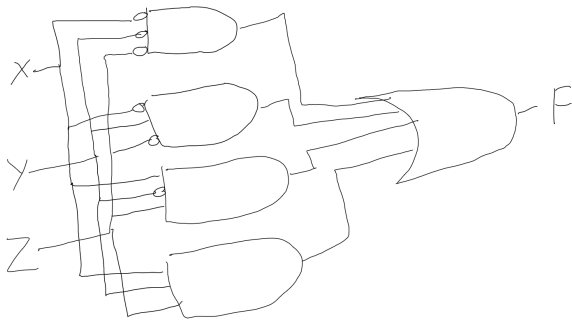b) Draw the logic diagram using the original Boolean expression.



c) Simplify using Boolean algebra.

$$F = x'y'z' + x'yz' + xy'z + xyz$$


$$F = (y' + y)(x'z' + xz)$$

$$F = (x'z' + xz)$$

- d) List the truth table of the simplified expression and show it is equivalent to the original.

| x | y | z | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

- e) Draw the logic diagram of the simplified function and compare the total number of gates to part (b).
3 Gates vs 5 Gates

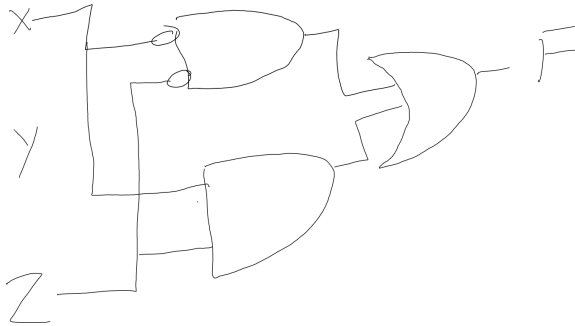


Question 5: (9 pts) Consider the following Boolean function: $F = A'B'C' + AB'C + ABC'$ For this question, do not use gates with inverted inputs. If you need an inverter, show it explicitly.

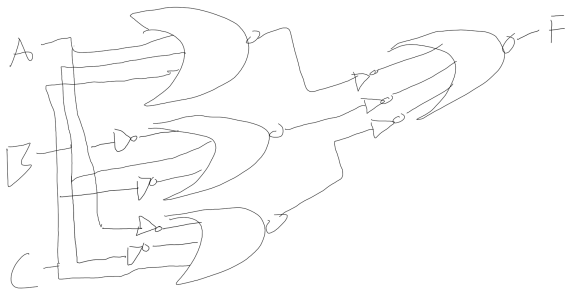- a) Implement it using only NOR gates and inverters? Draw the logic circuit. Assume your NOR gates can have up to four inputs.

$$F = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B \overline{C}$$

$$= \overline{\overline{\overline{A} \overline{B} \overline{C}} + \overline{\overline{\overline{A} \overline{B} C}} + \overline{\overline{\overline{A} B \overline{C}}}}$$



- b) Redraw the circuit using only 2-input NOR gates.
Hint: First, convert to 2-input gates. Then convert to NORs.


$$F = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B \overline{C}$$

$$= \overline{A} (\overline{B} + C) + \overline{A} ((\overline{B} + C) + (\overline{B} + C))$$

$$= \overline{\overline{A + (\overline{B} + C)}} + \overline{\overline{A + ((\overline{B} + C) + (\overline{B} + C)))}}$$

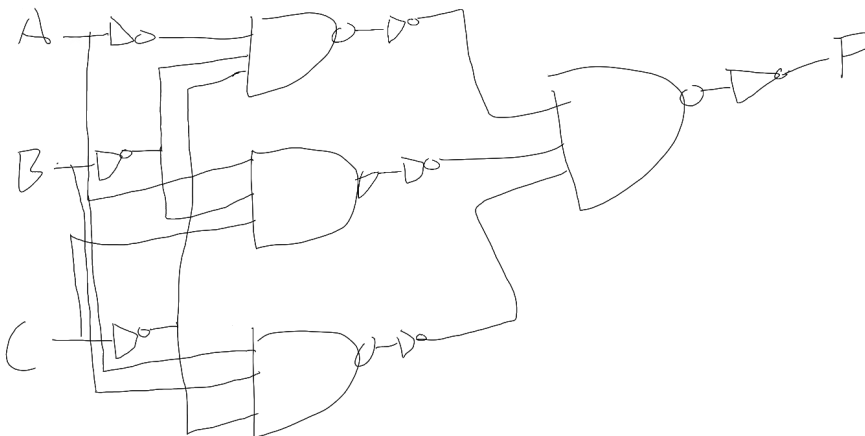- c) Now implement the function using only NAND gates with up to 4-inputs.


$$F = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B \overline{C} = (\overline{\overline{A} \overline{B} \overline{C}}) + (\overline{\overline{A} \overline{B} C}) + (\overline{\overline{A} B \overline{C}}) = ((\overline{\overline{A} \overline{B} \overline{C}}) (\overline{\overline{A} \overline{B} C}) (\overline{\overline{A} B \overline{C}}))$$



Question 6: (6 pts) Consider the following Boolean function: $F = (x + y + z') \bullet (x + y' + z) \bullet (x' + y' + z')$ For this question, do not use gates with inverted inputs. If you need an inverter, show it explicitly.

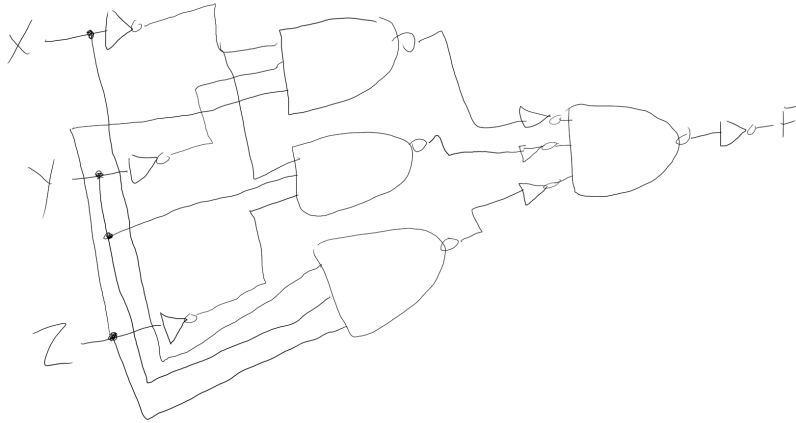- a) Implement it using only NAND gates and inverters? Draw the logic circuit. Assume your NAND gates can have up to four inputs.

$$\begin{aligned} F &= (x + y + z') \bullet (x + y' + z) \bullet (x' + y' + z') \\ &= \overline{(x'y'z)} \bullet \overline{(x'yz')} \bullet \overline{(xyz)} \\ &= \overline{\overline{\overline{(x'y'z)} \bullet \overline{(x'yz')} \bullet \overline{(xyz)}}} \end{aligned}$$



- b) Redraw the circuit using only 2-input NAND gates.
Hint: First, convert to 2-input gates. Then convert to NANDs.

Question 7: (3 pts) Derive a Boolean expression for the complement G' of the function $G(a, b, c) = a'bc' + a'c + ab'c'$. Simplify.

$$\begin{aligned}
 G(a, b, c) &= a'bc' + a'c + ab'c' \\
 \overline{G}(a, b, c) &= (a + b' + c)(a + c')(a' + b + c) \\
 &= (a + b' + c)(a + c')(a' + b + c) \\
 &= (a'b'c' + a'c' + ab + abc + abc' + bc' + ac + ab'c) \\
 &= (a'b'c' + a'c' + ab + bc' + ac + ab'c)
 \end{aligned}$$

GRADING SCALE

Total: 43 pts

| | | | | | | | | |
|--------------|----|---|----|----|----|----|----|----|
| Pts | 0 | 5 | 10 | 15 | 21 | 26 | 32 | 37 |
| Letter Grade | D- | D | C- | C | B- | B | A- | A |