

Homework 1

ECE3544 CRN:82989

Jacob Abel

August 27, 2018

Problem 1: Using 2's complement arithmetic, add the following decimal numbers, showing all work. i.e. perform $17 + 19$. Use the smallest number of bits possible to represent each number and the sum without overflow.


$$17 + 19 =$$

Problem 2: For the addition in problem 1, use one less bit to represent the numbers and show how the overflow can be detected.

Problem 3: Using the same guidelines as for problem 1, subtract decimal 87 from 37, i.e. perform $37 - 87$.

Problem 4: Give the hexadecimal representation of the answer to problem 3.

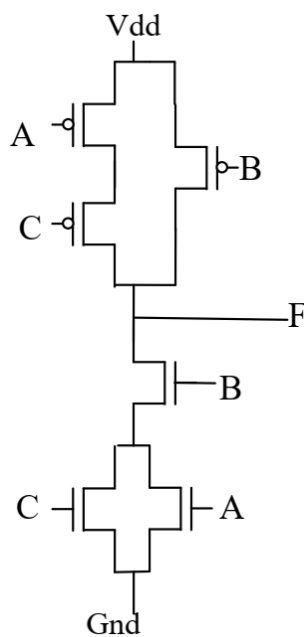Problem 5: Write the truth table and Boolean function implemented by the CMOS gate below.



A	B	C	F
0	0	0	
0	0	1	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	
1	1	0	
1	1	1	

Problem 6: Draw transistor schematics of a CMOS gate for each of the following Boolean functions:

a) $F = \overline{(W + Z) \cdot (Y + X)}$

b) $G = \overline{(B + C + D) \cdot A}$

Problem 7: Which would you expect to have a bigger effect on the power consumed by a CMOS circuit, a 5% increase in the power supply voltage (V_{dd}) or a 10% increase in total capacitance? Briefly explain your answer.