


Homework 4

ECE2004 CRN:12898

Jacob Abel

March 2, 2018

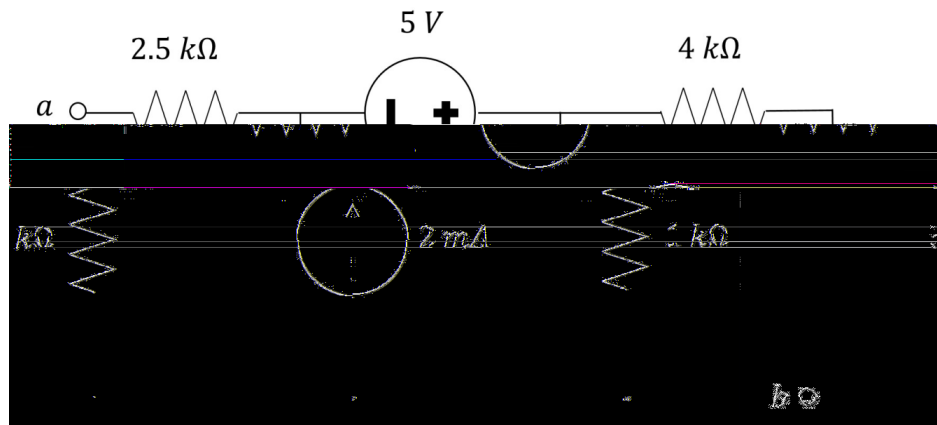Question 1: Find the Thevenin equivalent voltage and resistance at terminals $a - b$.




Closed

Open


$$\begin{aligned}
 R_{5V} &= 4k\Omega + 1k\Omega + 2.5k\Omega \parallel 5k\Omega = 6670\Omega & V_{ab5V} &= V_{5k\Omega 5V} \\
 I_{ab5V} &= \frac{5V}{2.5k\Omega} \times \frac{2.5k\Omega \parallel 5k\Omega}{6670\Omega} = 0.5mA & V_{5k\Omega 5V} &= 5V \frac{5k\Omega}{5k\Omega + 4k\Omega + 1k\Omega} = 2.5V \\
 R_{2mA} &= (4k\Omega + 1k\Omega) \parallel 5k\Omega \parallel 2.5k\Omega = 1250\Omega & V_{ab2mA} &= V_{5k\Omega 2mA} \\
 V_{ab2mA} &= 2mA \times 1250\Omega = 2.5V & V_{5k\Omega 2mA} &= 2mA \frac{1}{\frac{1}{5k\Omega} + \frac{1}{4k\Omega + 1k\Omega}} = 5V \\
 I_{ab2mA} &= \frac{2.5V}{2.5k\Omega} = 1mA & V_{ab} &= 5V - 2.5V = 2.5V \\
 I_{ab} &= 1mA - 0.5mA = 0.5mA
 \end{aligned}$$

$$\begin{aligned}
 V_{Th} &= 2.5V \\
 R_{Th} &= \frac{V_{ab}}{I_{ab}} = \frac{2.5V}{0.5mA} = 5k\Omega
 \end{aligned}$$

Question 2: Find the Norton equivalent current and resistance at terminals $a - b$.

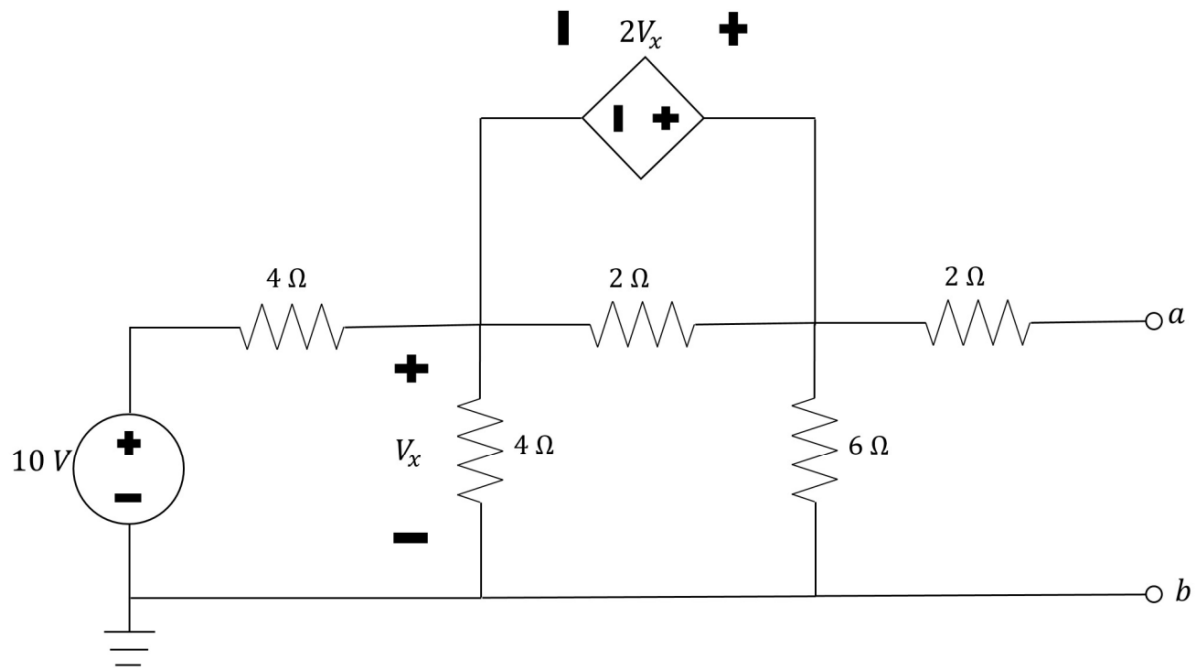

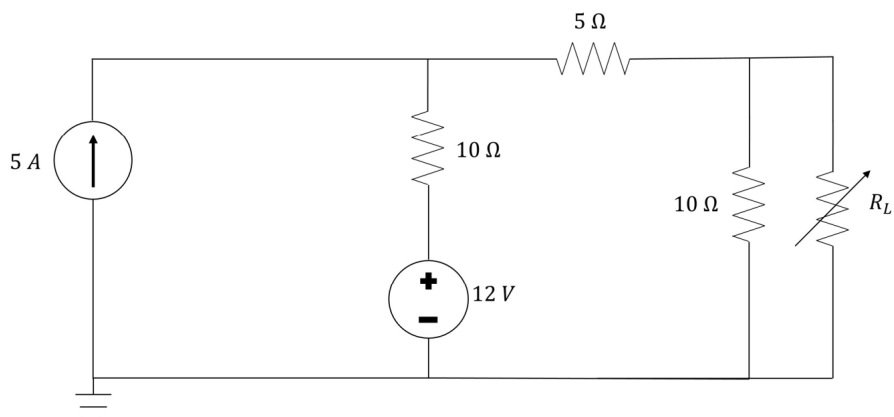Question 3: What is the maximum power that can be delivered to R_L ?



Open


Closed

$$\begin{aligned}
 R_{12V} &= 10\Omega + 5\Omega + 10\Omega = 25\Omega \\
 V_{R_L 12V} &= V_{10\Omega 12V} \\
 V_{10\Omega 12V} &= 12V \frac{10\Omega}{25\Omega} = 4.8V \\
 R_{5A} &= 10\Omega \parallel (5\Omega + 10\Omega) = 6\Omega \\
 V_{R_L 5A} &= V_{10\Omega 5A} \\
 V_{10\Omega 5A} &= 5A \times 6\Omega \frac{10\Omega}{5\Omega + 10\Omega} = 20V \\
 V_{R_L} &= 20V + 4.8V = 24.8V
 \end{aligned}$$

$$\begin{aligned}
 R_{12V} &= 10\Omega + 5\Omega = 15\Omega \\
 I_{R_L 12V} &= \frac{12V}{15\Omega} = 0.8A \\
 R_{5A} &= 10\Omega \parallel 5\Omega = \frac{10}{3}\Omega \\
 I_{R_L 5A} &= 5A \frac{10\Omega}{15\Omega} = \frac{10}{3}A \\
 I_{R_L} &= 0.8A + \frac{10}{3}A = \frac{62}{15}A \approx 4.13A
 \end{aligned}$$

$$\begin{aligned}
 V_{Th} &= 24.8V \\
 R_{Th} &= \frac{V_{ab}}{I_{ab}} = \frac{24.8V}{\frac{62}{15}A} = 6\Omega
 \end{aligned}$$

Question 4:

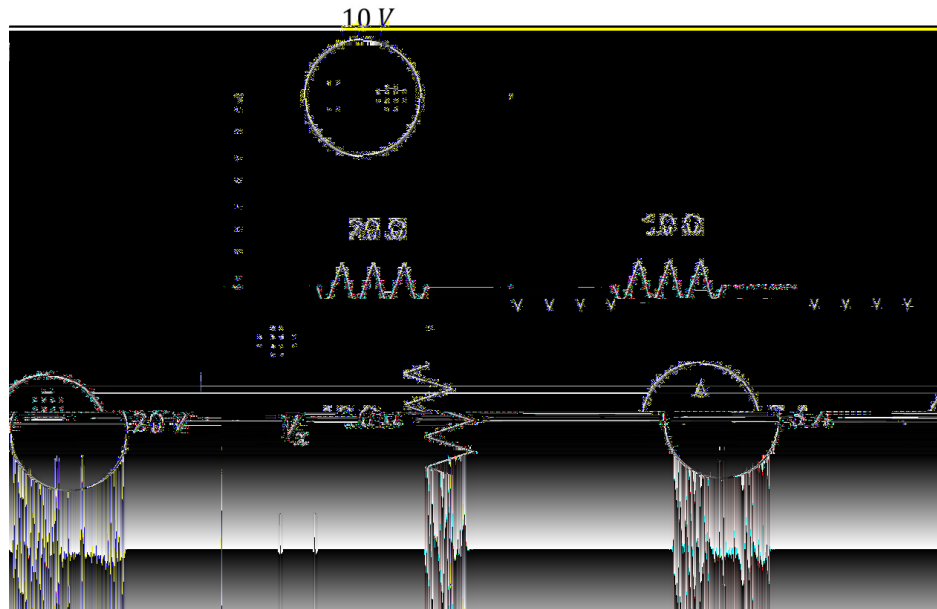

A) Use superposition to find V_x .

$$R_{20V} = 10\Omega + 10\Omega = 20\Omega$$

$$V_x = 20V \frac{10\Omega}{20\Omega} = 10V$$

$$V_{10\Omega} = 20V - 10V = 10V$$

$$V_{20\Omega} = 0V$$

$$R_{10V} = \frac{1}{\frac{1}{20\Omega} + \frac{1}{10\Omega + 10\Omega}} = 10\Omega$$

$$V_{20\Omega} = 10V$$

$$V_x = 10V \frac{10\Omega}{20\Omega} = 5V$$

$$V_{10\Omega} = 10V - 5V = 5V$$

$$R_{3A} = \frac{1}{\frac{1}{10\Omega} + \frac{1}{10\Omega}} = 5\Omega$$

$$V_{20\Omega} = 0V$$

$$V_x = 10\Omega \times 3A \times \frac{1}{2} = 15V$$

$$V_{10\Omega} = 15V$$

$$V_x = 10V - 5V + 15V = 20V$$

B) Analyse the full circuit with mesh current or nodal analysis to find V_x .