

Design & Simulate 14

ECE2204 CRN:82929

Jacob Abel


October 2, 2018

Problem 14.10-8.a.1:


Switched from NMOS to PMOS.

Design

Design a MOSFET current source circuit to meet the following specifications. The circuit to be designed has the configuration shown below with all NMOS transistors swapped with PMOS transistors and V^+ swaps places with V^- . The bias voltages are $V^+ = 2.5V$ and $V^- = 0$. Transistors are available with parameters $k'_p = 100\mu A/V^2$, $V_{TP} = 0.4V$, and $\lambda = 0$. Design the circuit such that $I_{REF} = 100\mu A$, $I_O = 60\mu A$, and $V_{SD2}(sat) = 0.4V$.

 

(Original)

 

(w/ PMOS and Voltage Inversion)

$$V_{SD2}(sat) = V_{SG2} + V_{TP}$$

$$V_{SG2} = V_{SG1} = V_{SD2}(sat) - V_{TP} = 0.4V + 0.4V = 0.8V$$

$$\frac{W}{L}_2 = \frac{2I_O}{k'_p(V_{SG2} + V_{TP})^2} = \frac{2(60\mu A)}{(100\mu A/V^2)(0.8V - 0.4V)^2} = 7.5$$

$$\frac{W}{L}_1 = \frac{2I_{REF}}{k'_p(V_{SG1} + V_{TP})^2} = \frac{2(100\mu A)}{(100\mu A/V^2)(0.8V - 0.4V)^2} = 12$$


$$V_{SG3} = V^+ - V^- - V_{GS1} = 2.5V - 0V - 0.8V = 1.7V$$

$$\frac{W}{L}_3 = \frac{2I_{REF}}{k'_p(V_{SG3} + V_{TP})^2} = \frac{2(100\mu A)}{(100\mu A/V^2)(1.7V - 0.4V)^2} = 1.183$$

The final design values are $\frac{W}{L}_1 = 12$, $\frac{W}{L}_2 = 7.5$, and $\frac{W}{L}_3 = 1.183$.

Validation

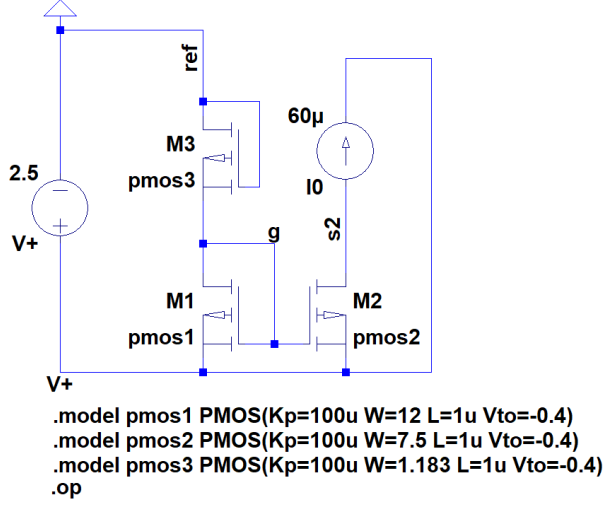LTSpice Implementation (values within < 1%)



| | | |
|---------|---------------|----------------|
| V(g): | 1.69378 | voltage |
| V(v+): | 2.5 | voltage |
| V(s2): | 2.5 | voltage |
| Id(M2): | -5.99248e-005 | device_current |
| Ig(M2): | -0 | device_current |
| Ib(M2): | 2.72735e-019 | device_current |
| Is(M2): | 5.99248e-005 | device_current |
| Id(M1): | -99.0091 | device_current |
| Ig(M1): | -0 | device_current |
| Ib(M1): | 8.16221e-013 | device_current |
| Is(M1): | 99.0091 | device_current |
| Id(M3): | -99.0091 | device_current |
| Ig(M3): | -0 | device_current |
| Ib(M3): | 1.70378e-012 | device_current |
| Is(M3): | 99.0091 | device_current |
| I(I0): | 6e-005 | device_current |
| I(V+): | -99.0091 | device_current |

$$Err_{V_{SG1}} = \frac{|1.7 - 1.69378|}{1.7} = 0.0037 = 0.37\%$$

$$Err_{I_{REF}} = \frac{|100 - 99.0091|}{100} = 0.0099 = 0.99\%$$

$$Err_{I_O} = \frac{|60 - 59.9248|}{60} = 0.00125 = 0.13\%$$

Problem 14.10-8.b.1:

Derived from Problem 10.54 from page 744 of the textbook by changing some values and adding a 5th transistor.


Design

The transistor circuit shown to the left is biased at $V^+ = 12V$ and $V^- = 0V$. The transistor parameters are $V_{TP} = -1.2V$, $k'_p = 80\mu A/V^2$, $\lambda = 0$, $\frac{W}{L}_1 = \frac{W}{L}_2 = 25$, and $\frac{W}{L}_3 = \frac{W}{L}_4 = \frac{W}{L}_5 = 4$. Determine I_{REF} , I_O , and $V_{SD2}(sat)$.

$$V_{SG1} = V_{SG2}, V_{GD1} = V_{GD2} = V_{GD3} = V_{GD4} = V_{GD5} = 0V$$

$$\begin{aligned} V^+ &= V_{SG1} + V_{SG3} + V_{SG4} + V_{SG5} \\ \Rightarrow V_{SG3} + V_{SG4} + V_{SG5} &= 3V_{SG3} \\ \Rightarrow V_{SG1} &= V^+ - 3V_{SG3} \end{aligned}$$

 Ran out of time and was unable to complete the second problem.



This assignment should demonstrate a basic understanding of designing basic MOSFET circuits by adapting the widths and lengths of the transistors.

I have neither given nor received unauthorized assistance on this assignment.