


# Homework 3

ECE2504 CRN:82729

Jacob Abel

September 17, 2017

**Question 1:** (6 pts)

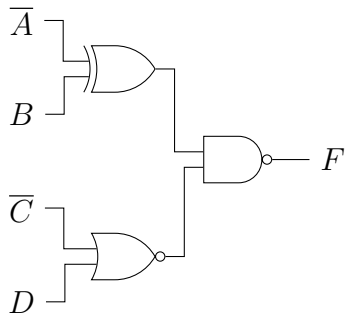

a) Write the logic equation for the variable F in the circuit below, as implemented.

$$F = (\overline{A} \oplus B)(\overline{\overline{C} + D})$$

b) Complete the truth table.

A	B	C	D	$\overline{A} \oplus B$	$\overline{\overline{A} + B}$	F
0	0	0	0	1	0	1
0	0	0	1	1	0	1
0	0	1	0	1	1	0
0	0	1	1	1	0	1
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	0	1	1
0	1	1	1	0	0	1
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	1
1	0	1	1	0	0	1
1	1	0	0	1	0	1
1	1	0	1	1	0	1
1	1	1	0	1	1	0
1	1	1	1	1	0	1

A	B	$\overline{A} \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

A	B	$\overline{A} \oplus B$
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$\overline{\overline{A} + B}$
0	0	0
0	1	0
1	0	1
1	1	0

- c) Find an equivalent expression in sum-of-products form. (Hint: you can check your result by verifying that the truth table remains the same.)

$$F(A, B, C, D) = \Sigma m(0, 1, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 15)$$

$$\begin{aligned} F(A, B, C, D) = & \bar{A} \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} \bar{B} C \bar{D} + \bar{A} \bar{B} C D + \bar{A} B \bar{C} \bar{D} + \bar{A} B \bar{C} D \\ & + \bar{A} B C \bar{D} + \bar{A} B C D + A \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} D + A \bar{B} C \bar{D} + A \bar{B} C D \\ & + A B \bar{C} \bar{D} + A B \bar{C} D + A B C \bar{D} \end{aligned}$$

$$\begin{aligned} F(A, B, C, D) = & \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} D + A \bar{B} \bar{C} D + \bar{A} \bar{B} C \bar{D} + A \bar{B} C \bar{D} \\ & + \bar{A} B \bar{C} \bar{D} + A B \bar{C} \bar{D} + \bar{A} B \bar{C} D + A B \bar{C} D + \bar{A} B C \bar{D} \\ & + A B C \bar{D} + A \bar{B} C \bar{D} + \bar{A} B C \bar{D} \end{aligned}$$

$$\begin{aligned} F(A, B, C, D) = & (\bar{A} + A)(\bar{B} \bar{C} \bar{D} + \bar{B} \bar{C} D + \bar{B} C \bar{D} + B \bar{C} \bar{D} + B \bar{C} D + B C \bar{D}) \\ & + A \bar{B} C \bar{D} + \bar{A} B C \bar{D} \end{aligned}$$

$$\begin{aligned} F(A, B, C, D) = & \bar{B} \bar{C} \bar{D} + B \bar{C} \bar{D} + \bar{B} \bar{C} D + B \bar{C} D + \bar{B} C \bar{D} + B C \bar{D} \\ & + A \bar{B} C \bar{D} + \bar{A} B C \bar{D} \end{aligned}$$


$$F(A, B, C, D) = (\bar{B} + B)(\bar{C} \bar{D} + \bar{C} D + C \bar{D}) + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

$$F(A, B, C, D) = \bar{C} \bar{D} + C \bar{D} + \bar{C} D + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

$$F(A, B, C, D) = (\bar{C} + C)(\bar{D}) + \bar{C} \bar{D} + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

$$F(A, B, C, D) = D + \bar{C} \bar{D} + A \bar{B} C \bar{D} + \bar{A} B C \bar{D}$$

**Question 2:** (6 pts)

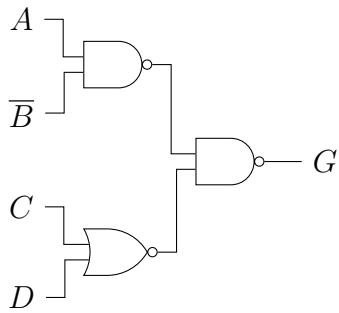

- a) Write the logic equation for the variable F in the circuit below, as implemented.

$$G = \overline{\overline{A\overline{B}}} \overline{\overline{C + D}}$$

- b) Complete the truth table.

A	B	C	D	$\overline{\overline{A\overline{B}}}$	$\overline{\overline{C + D}}$	G
0	0	0	0	1	1	0
0	0	0	1	1	0	1
0	0	1	0	1	0	1
0	0	1	1	1	0	1
0	1	0	0	1	1	0
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	0	1	1
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	0	0	1
1	1	0	0	1	1	0
1	1	0	1	1	0	1
1	1	1	0	1	0	1
1	1	1	1	1	0	1

A	B	$\overline{\overline{A\overline{B}}}$
0	0	1
0	1	1
1	0	0
1	1	1

A	B	$\overline{A\overline{B}}$
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$\overline{\overline{A + B}}$
0	0	1
0	1	0
1	0	0
1	1	0

- c) Find an equivalent expression in product-of-sums form. (Hint: you can check your result by verifying that the truth table remains the same.)

$$G(A, B, C, D) = \Pi m(0, 4, 12)$$

$$G(A, B, C, D) = (A + B + C + D)(A + \overline{B} + C + D)(\overline{A} + \overline{B} + C + D)$$

$$G(A, B, C, D) = (AB' + AC + AD + BA' + BC + C + CD + D)(A + \overline{B} + C + D)$$

$$G(A, B, C, D) = (AB' + AC + AD + ACD + B'D + A'BC + C + CD + A'BD + D)$$

**Question 3:** (3 pts) Use Boolean algebra to prove that  $wxy' + xy'z' + xy + y'z = x + y'z$

$$wx\bar{y} + x\bar{y}\bar{z} + xy + \bar{y}z = x + \bar{y}z$$

$$x\bar{y}(w + \bar{z}) + xy + \bar{y}z = x + \bar{y}z$$

$$(\bar{y} + y)(x(w + \bar{z}) + 1) + \bar{y}z = x + \bar{y}z$$


$$x + \bar{y}z = x + \bar{y}z$$

**Question 4:** (10 pts) Given the Boolean function  $F = x'y'z' + x'yz' + xy'z + xyz$

a) List the truth table.

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

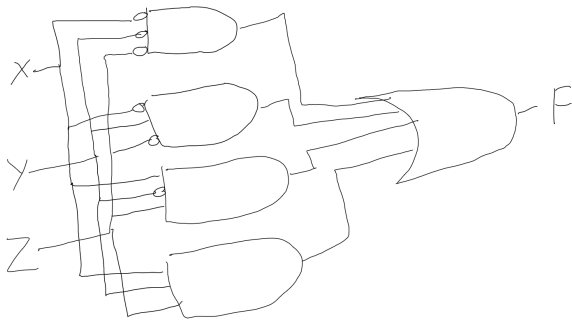b) Draw the logic diagram using the original Boolean expression.



c) Simplify using Boolean algebra.

$$F = x'y'z' + x'yz' + xy'z + xyz$$


$$F = (y' + y)(x'z' + xz)$$

$$F = (x'z' + xz)$$

- d) List the truth table of the simplified expression and show it is equivalent to the original.

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- e) Draw the logic diagram of the simplified function and compare the total number of gates to part (b).  
3 Gates vs 5 Gates

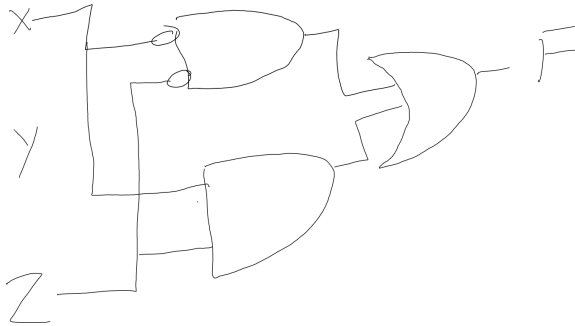



**Question 5:** (9 pts) Consider the following Boolean function:  $F = A'B'C' + AB'C + ABC'$  For this question, do not use gates with inverted inputs. If you need an inverter, show it explicitly.

- a) Implement it using only NOR gates and inverters? Draw the logic circuit. Assume your NOR gates can have up to four inputs.

$$F = \overline{A} \overline{B} \overline{C} + A \overline{B} C + A B \overline{C}$$

$$= \overline{\overline{\overline{A} \overline{B} \overline{C}} + \overline{\overline{A \overline{B} C}} + \overline{\overline{A B \overline{C}}}}$$



- b) Redraw the circuit using only 2-input NOR gates.  
Hint: First, convert to 2-input gates. Then convert to NORs.


$$F = \overline{A} \overline{B} \overline{C} + A \overline{B} C + A B \overline{C}$$

$$= \overline{A} (\overline{B + C}) + A ((\overline{B + C}) + (\overline{B + C}))$$

$$= \overline{A + (\overline{B + C})} + (\overline{A + ((\overline{B + C}) + (\overline{B + C})))})$$

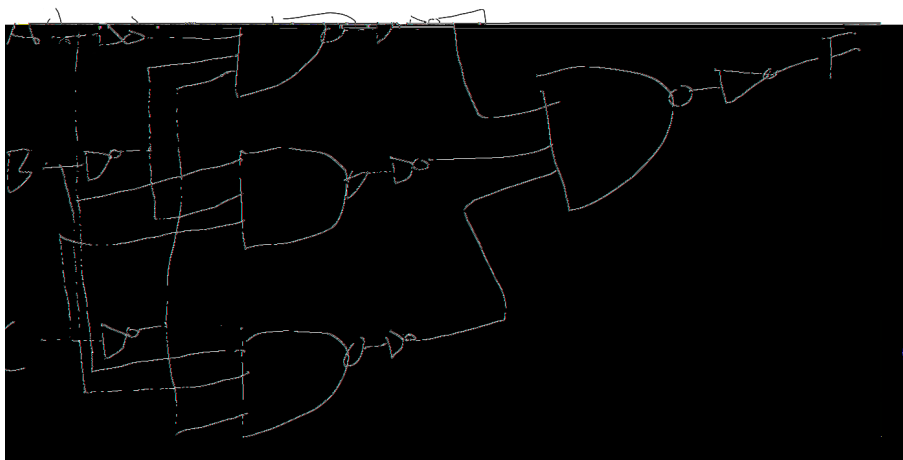- c) Now implement the function using only NAND gates with up to 4-inputs.

$$F = \overline{A} \overline{B} \overline{C} + A \overline{B} C + A B \overline{C} = (\overline{\overline{A} \overline{B} \overline{C}}) + (\overline{\overline{A \overline{B} C}}) + (\overline{\overline{A B \overline{C}}}) = ((\overline{\overline{A} \overline{B} \overline{C}}) (\overline{\overline{A \overline{B} C}}) (\overline{\overline{A B \overline{C}}}))$$



**Question 6:** (6 pts) Consider the following Boolean function:  $F = (x + y + z') \bullet (x + y' + z) \bullet (x' + y' + z')$  For this question, do not use gates with inverted inputs. If you need an inverter, show it explicitly.

- a) Implement it using only NAND gates and inverters? Draw the logic circuit. Assume your NAND gates can have up to four inputs.

$$\begin{aligned} F &= (x + y + z') \bullet (x + y' + z) \bullet (x' + y' + z') \\ &= \overline{(x'y'z)} \bullet \overline{(x'yz')} \bullet \overline{(xyz)} \\ &= \overline{\overline{\overline{(x'y'z)} \bullet \overline{(x'yz')} \bullet \overline{(xyz)}}} \end{aligned}$$



- b) Redraw the circuit using only 2-input NAND gates.  
Hint: First, convert to 2-input gates. Then convert to NANDs.

**Question 7:** (3 pts) Derive a Boolean expression for the complement  $G'$  of the function  $G(a, b, c) = a'bc' + a'c + ab'c'$ . Simplify.

$$\begin{aligned}
 G(a, b, c) &= a'bc' + a'c + ab'c' \\
 \overline{G}(a, b, c) &= (a + b' + c)(a + c')(a' + b + c) \\
 &= (a + b' + c)(a + c')(a' + b + c) \\
 &= (a'b'c' + a'c' + ab + abc + abc' + bc' + ac + ab'c) \\
 &= (a'b'c' + a'c' + ab + bc' + ac + ab'c)
 \end{aligned}$$

#### GRADING SCALE

Total: 43 pts

Pts	0	5	10	15	21	26	32	37
Letter Grade	D-	D	C-	C	B-	B	A-	A