

Design & Simulate 8

ECE2204 CRN:82929

Jacob Abel


September 12, 2018

Problem 8.2-11.a.1:

The circuit was a random circuit I threw together in LTSpice.


Design

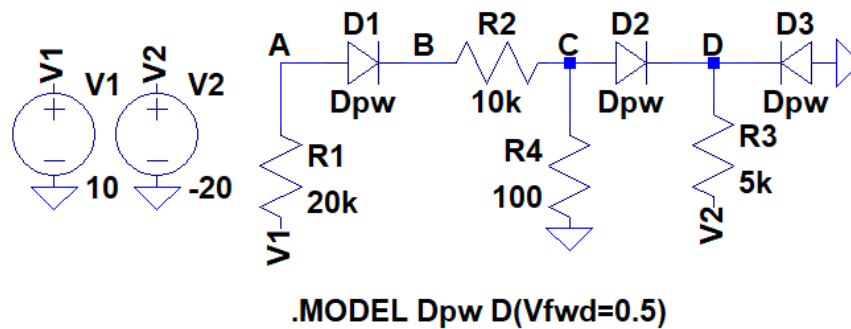Using the circuit displayed below, determine the current flowing through D_1 , D_2 , D_3 and the voltage at points A, B, C, and D.



Validation

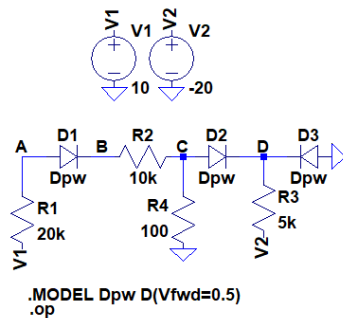LTSpice Implementation (accurate with $< 1\%$ deviation from design result)



V(a):	3.66666	voltage
V(v1):	10	voltage
V(d):	-0.500004	voltage
V(v2):	-20	voltage
V(b):	3.16666	voltage
V(c):	-3.2666e-006	voltage
I(D3):	0.0035833	device_current
I(D2):	0.000316699	device_current
I(D1):	0.000316667	device_current
I(R4):	3.2666e-008	device_current
I(R2):	-0.000316667	device_current
I(R3):	0.0039	device_current
I(R1):	-0.000316667	device_current
I(V2):	0.0039	device_current
I(V1):	-0.000316667	device_current

$$Err_{V_R} = \frac{|17 - 16.966|}{17} = 0.002 = 0.2\%$$

$$Err_{i_D(\text{peak})} = \frac{|31.35 - 31.30|}{31.35} = 0.0015 = 0.15\%$$

$$Err_{\%t} = \frac{|0.3416 - \frac{151.7 - 27.9}{360}|}{34.16} = 0.000007 = 0.00\%$$


$$Err_{Avg} = \frac{0.20 + 0.15 + 0.00}{3} = 0.12\%$$

Problem 8.2-5.b.1:

Derived by swapping the independent/dependent state of P_Z and $I_L(\max)$ and by changing the values.

Design

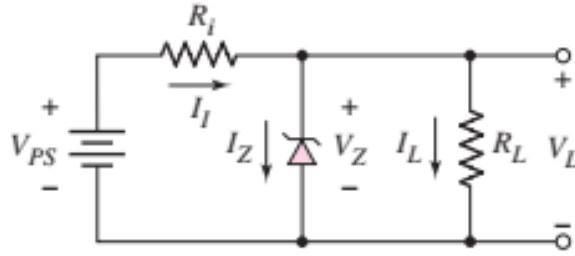Design a voltage regulator using the circuit shown below. The voltage regulator is to power a car radio at $V_L = 10V$ from an automobile battery whose voltage may vary between 14 and 19V. The current in the radio will vary between 0 (off) to some unknown $I_L(\max)$ at full volume. The Zener diode has a maximum power rating of $P_Z(\max) = 1W$.



$$V_Z = V_{\text{radio}} = 2.5V \quad (1)$$

$$I_Z(\max) = \frac{P_Z}{V_Z} = \frac{1W}{10V} = 0.1A \quad (2)$$

$$I_Z(\max) = \frac{I_L(\max)[V_{PS}(\max) - V_Z] - I_L(\min)[V_{PS}(\min)]}{V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)} \quad (3)$$

$$\Rightarrow I_L(\max) = \frac{I_Z(\max)[V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)] + I_L(\min)[V_{PS}(\min)]}{V_{PS}(\max) - V_Z} \quad (4)$$

$$= \frac{0.1A[14V - 0.9 \times 10V - 0.1 \times 19V]}{19V - 10V} \quad (5)$$

$$= 34.44mA \quad (6)$$


$$R_i = \frac{V_{PS}(\max) - V_Z}{I_Z(\max) + I_L(\min)} = \frac{19V - 10V}{0.1A + 0} = 90\Omega \quad (7)$$

$$P_{R_i}(\max) = \frac{(V_{PS}(\max) - V_Z)^2}{R_i} = \frac{(19V - 10V)^2}{90\Omega} = 0.9W \quad (8)$$

$$I_Z(\min) = \frac{V_{PS}(\min) - V_Z}{R_i} - I_L(\max) = \frac{14V - 10V}{90\Omega} - 34.44mA = 10mA \quad (9)$$

Validation

LTSpice Implementation

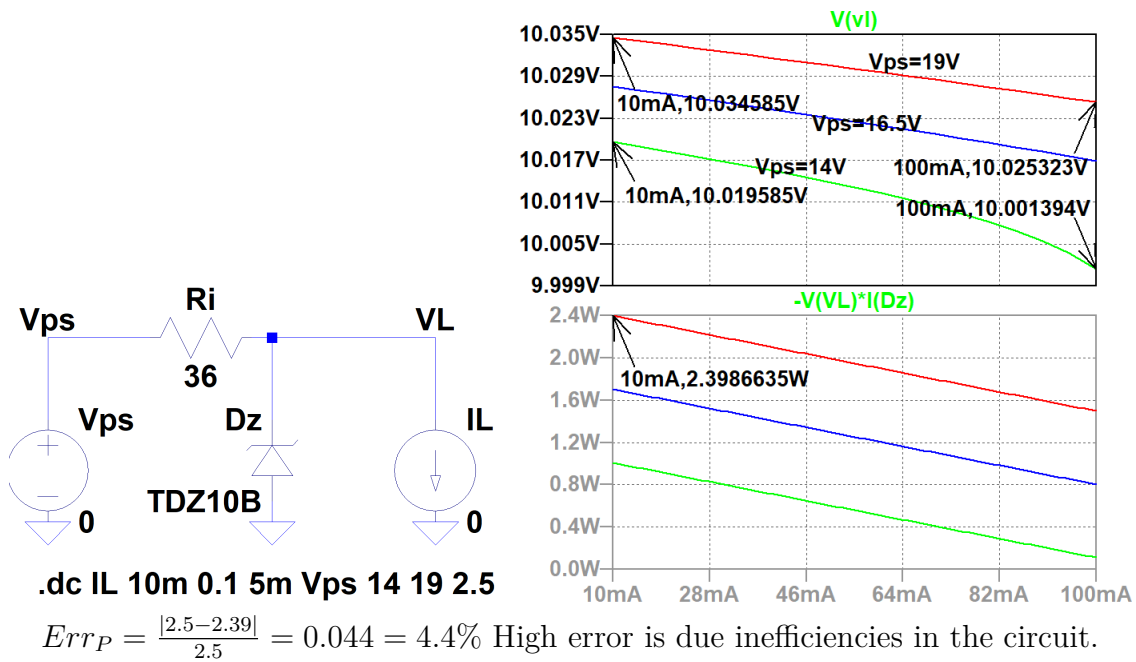

This assignment should demonstrate a basic understanding of manipulating zener diode voltage regulator circuits and solving multiple diode circuits.

I have neither given nor received unauthorized assistance on this assignment.