


Homework 1

ECE2004 CRN:12898

Jacob Abel

January 29, 2018

Question 1:

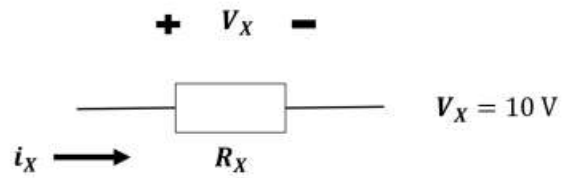


A. The power absorbed by this element is -100 mW. Find R_x and i_x .

$$i_x = \frac{P}{V} = \frac{-100\text{mW}}{10\text{V}} = -0.01\text{A}$$
$$R_x = \frac{V^2}{P} = \frac{(10\text{V})^2}{-100\text{mW}} = -1000\Omega$$

B. Which direction is the current i_x flowing? From negative to positive.

C. Is this element producing or consuming power? It is producing power.

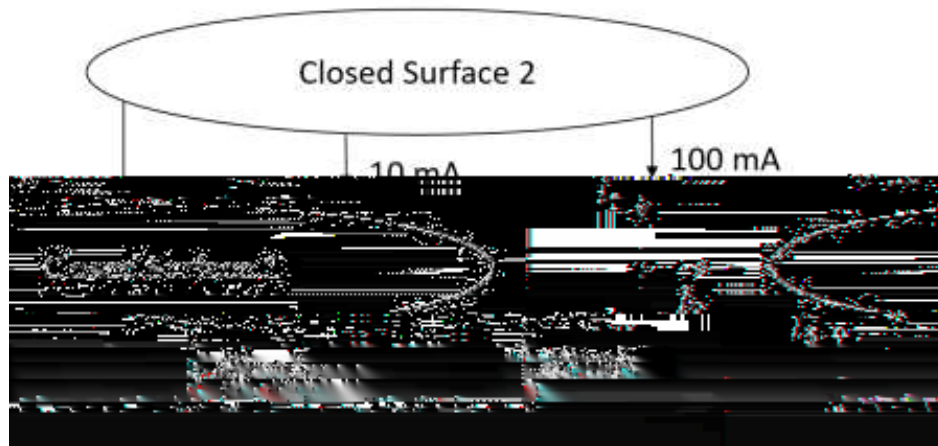Question 2: KCL states current entering a node is equal to current leaving a node. There is, however, no reason to restrict ourselves to simply nodes. It may be restated as currents entering a closed surface have to equal currents leaving a closed surface. That being said, solve for the currents (I_1, I_2, I_3) .



$$\begin{aligned}\text{Closed Surface 1} &= -40mA + 30mA + 100mA + 10mA - I_2 \\ &= 0.1A - I_2\end{aligned}$$

$$I_2 = 0.1A$$

$$\text{Closed Surface 2} = -10mA - 100mA - I_1$$

$$I_1 = -0.11A$$

$$I_1 + I_2 + I_3 = 0$$


$$I_3 = -I_1 - I_2$$

$$I_3 = 0.11A - 0.1A$$

$$I_3 = 0.01A$$

$$(I_1, I_2, I_3) = (-0.11A, 0.1A, 0.01A)$$

Question 3:

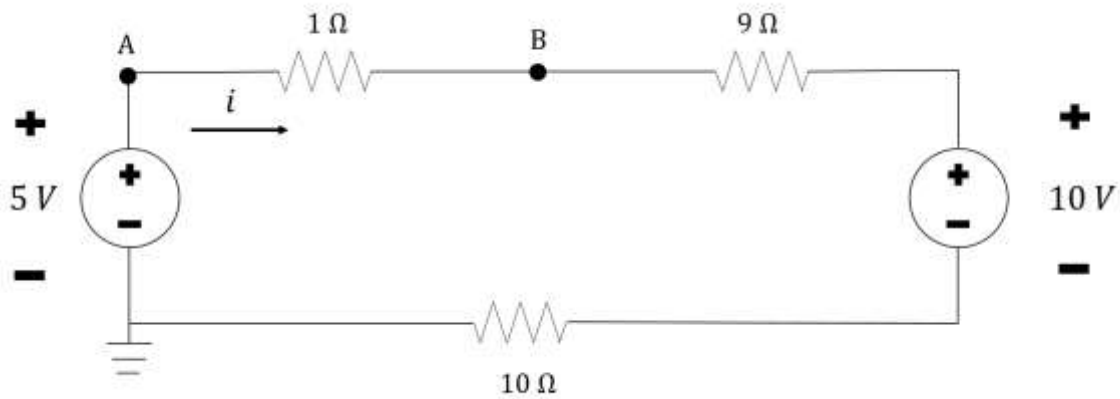

A. Find the current i .

$$-5V + v_{1\Omega} + v_{9\Omega} + 10V + v_{10\Omega} = 0$$

$$v_{1\Omega} + v_{9\Omega} + v_{10\Omega} = -5V$$

$$1\Omega \times i + 9\Omega \times i + 10\Omega \times i = -5V$$

$$20\Omega \times i = -5V$$


$$i = \frac{-5V}{20\Omega}$$

$$i = -0.25A$$

B. Find V_{AB} , the voltage across the 1Ω resistor. $V_{AB} = 1\Omega \times -0.25A = -0.25V$

C. Is the voltage at node B higher or lower than the voltage at node A? The voltage is higher at node A than at node B as the potential difference V_{AB} is negative indicating that the voltage is decreasing as you approach B from A.

Question 4:

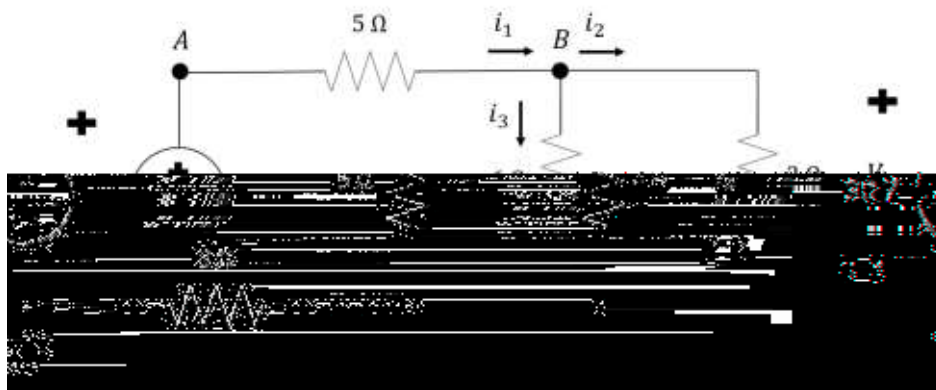

A. Solve for the current (i_1, i_2, i_3) as well as V_x .

$$-30V + i_1 \times (5\Omega + 3\Omega + \frac{1}{\frac{1}{6\Omega} + \frac{1}{3\Omega}}) = 0$$

$$i_1 \times (5\Omega + 3\Omega + 2\Omega) = 30V$$

$$i_1 = \frac{30V}{10\Omega}$$

$$i_1 = 3A$$

$$i_2 = 3A \frac{2\Omega}{6\Omega}$$

$$i_2 = 1A$$

$$i_3 = 3A \frac{2\Omega}{3\Omega}$$

$$i_3 = 2A$$

$$i_1 - i_2 - i_3 = 0A$$

$$(i_1, i_2, i_3) = (3A, 1A, 2A)$$

B. What is the voltage across the 5Ω resistor (V_{AB})? $V_{AB} = 5\Omega \times 3A = 15V$