


Homework 5

ECE2004 CRN:12898

Jacob Abel

March 23, 2018

Question 1:

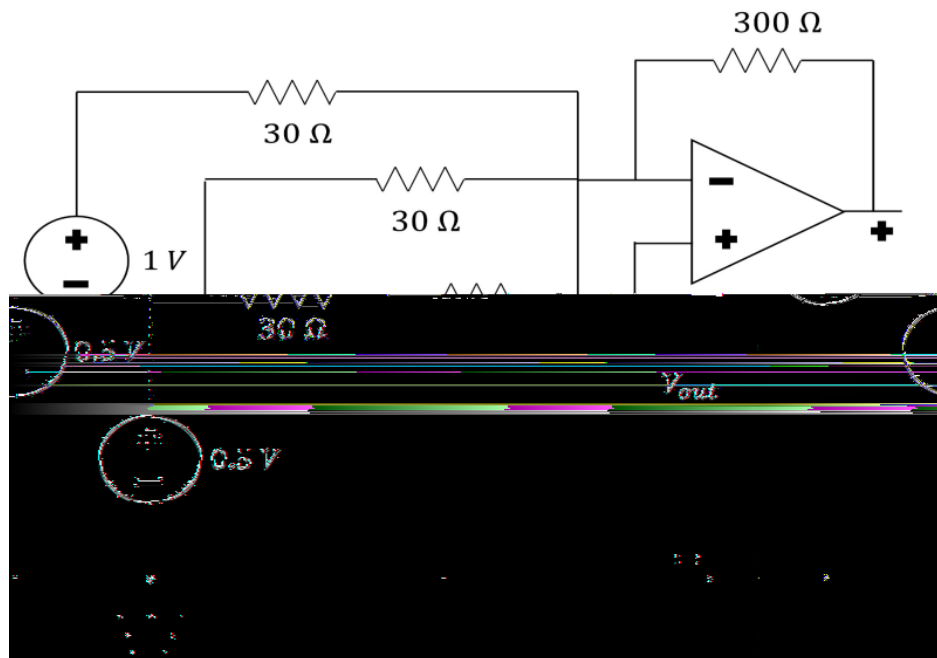


A) Solve for V_{out} .

$$V_{out} = -\frac{300\Omega}{30\Omega}(1V + 0.5V + 0.5V) = -20V$$

B) What type of amplifier circuit is this?

This is an inverting summing amplifier.

Question 2:

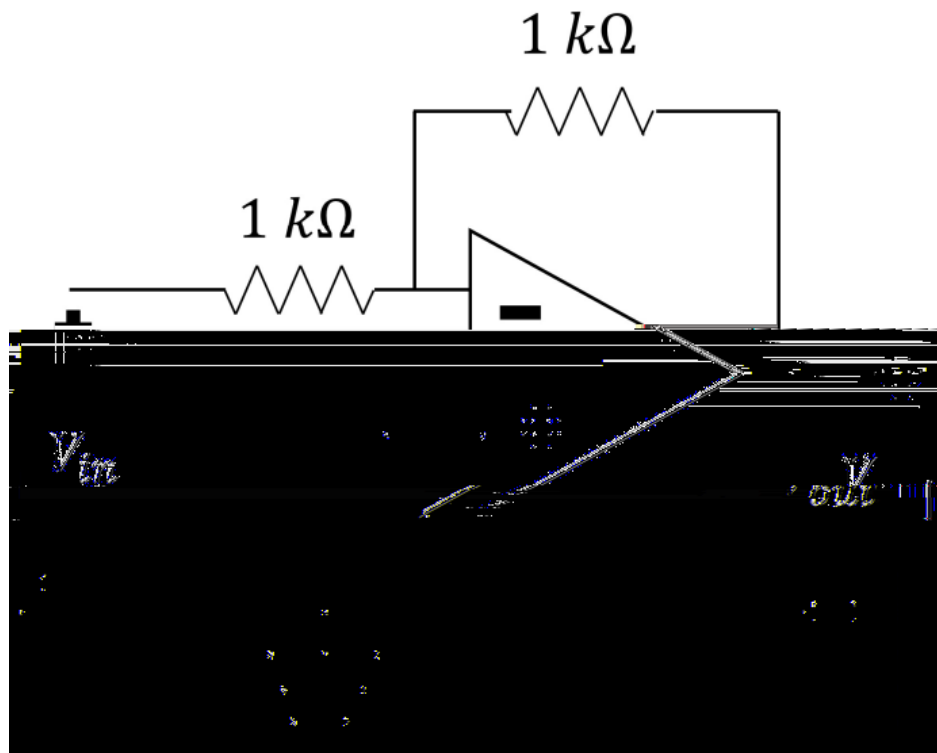


A) Solve for the gain of this circuit, $H = \frac{V_{out}}{V_{in}}$.

$$H = -\frac{1\text{ k}\Omega}{1\text{ k}\Omega} = -1$$

B) What type of circuit is this?

This is an inverting amplifier.

Question 3:

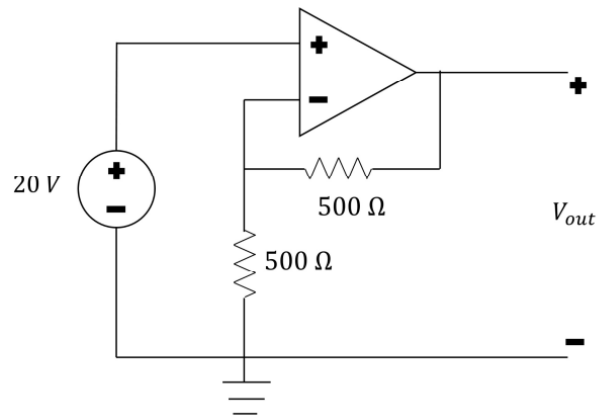


A) Solve for V_{out} .

$$V_{out} = \left(1 + \frac{500\Omega}{500\Omega}\right)20V = 40V$$

B) What type of amplifier circuit is this?

This is a non-inverting amplifier.

Question 4: Solve for V_{out} .

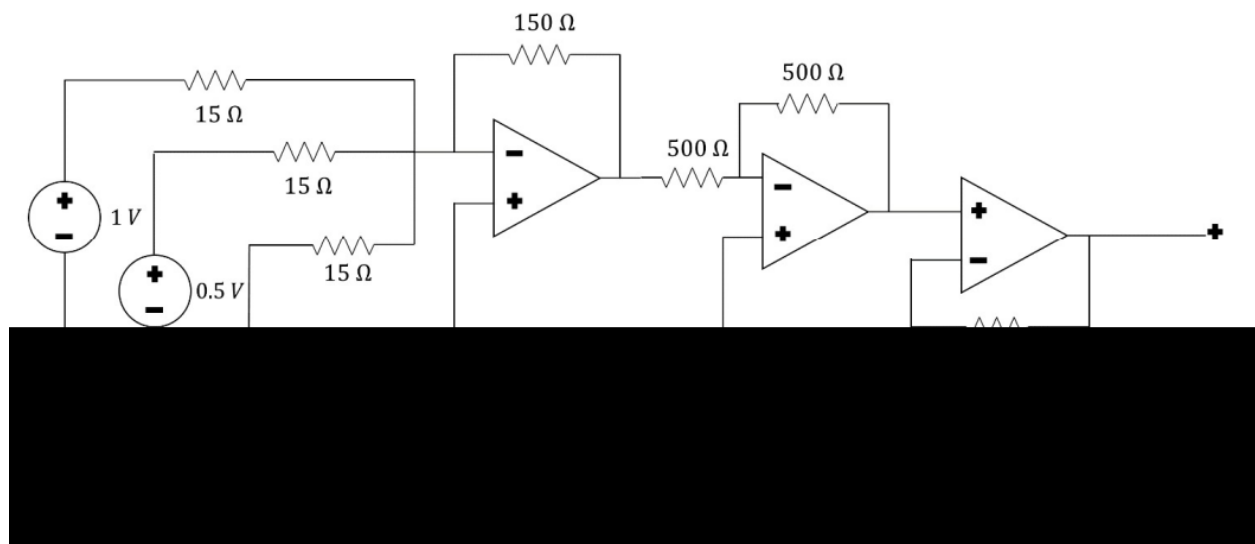

$$V_1 = \frac{150\Omega}{15\Omega}(1V + 0.5V + 0.5V) = -20V$$

$$V_2 = -\frac{500\Omega}{500\Omega} \times -20V = 20V$$

$$V_{out} = \left(1 + \frac{500\Omega}{500\Omega}\right)20V = 40V$$