

# Design & Simulate 18

ECE2204 CRN:82929

Jacob Abel


October 23, 2018

## Problem 19.16-11.a.1:
 
### Design

Design the all MOS inverter to bias the output at  $\frac{V_{SS}}{2}$  when the input is at  $\frac{V_{SS}}{2}$ . Assume  $V_{SS} = 5V$ ,  $V_{TP} = -1V$ ,  $V_{TN} = 1V$ ,  $k_p = k_n = 50\mu A/V^2$ ,  $i_D = 50\mu A$ ,  $I_{ref} = 100\mu A$ , and  $V_g = 0.75V$ .

At the bias, All transistors are in saturation.



$$i_D = \frac{k_n}{2} \frac{W}{L_1} \left( \frac{V_{SS}}{2} - V_{TN} \right)^2$$

$$\frac{W}{L_1} = \frac{i_D}{\frac{k_n}{2} \left( \frac{V_{SS}}{2} - V_{TN} \right)^2} = \frac{50\mu A}{\frac{50\mu A/V^2}{2} \left( \frac{5V}{2} - 1V \right)^2} = 0.8889$$

$$i_D = \frac{k_p}{2} \frac{W}{L_2} (V_{SS} - V_g + V_{TP})^2$$

$$\frac{W}{L_2} = \frac{i_D}{\frac{k_p}{2} (V_{SS} - V_g + V_{TP})^2} = \frac{50\mu A}{\frac{50\mu A/V^2}{2} (5V - 0.75V - 1V)^2} = 0.189$$

$$I_{ref} = \frac{k_p}{2} \frac{W}{L_3} (V_{SS} - V_g + V_{TP})^2$$

$$\frac{W}{L_3} = \frac{I_{ref}}{\frac{k_p}{2} (V_{SS} - V_g + V_{TP})^2} = \frac{100\mu A}{\frac{50\mu A/V^2}{2} (5V - 0.75V - 1V)^2} = 0.379$$

$$I_{ref} = \frac{k_n}{2} \frac{W}{L_4} (V_g - V_{TN})^2$$

$$\frac{W}{L_4} = \frac{I_{ref}}{\frac{k_n}{2} (V_g - V_{TN})^2} = \frac{100\mu A}{\frac{50\mu A/V^2}{2} (0.75V - 1V)^2} = 64$$

The circuit was designed with the following width ratios:

$$\frac{W}{L_1} = 0.8889, \frac{W}{L_2} = 0.189, \frac{W}{L_3} = 0.379, \frac{W}{L_4} = 64.$$

This problem should demonstrate a basic ability to manipulate, design, and analyse MOSFET based logic gates.

*I have neither given nor received unauthorized assistance on this assignment.*