


Homework 1

ECE2004 CRN:12898

Jacob Abel

January 29, 2018

Question 1:

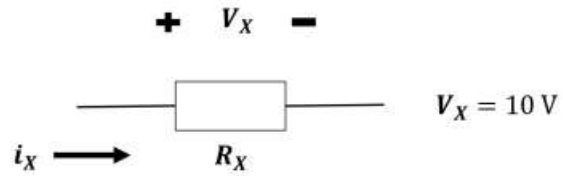


A. The power absorbed by this element is -100 mW . Find R_x and i_x .

$$i_x = \frac{P}{V} = \frac{-100\text{ mW}}{10\text{ V}} = -0.01\text{ A}$$
$$R_x = \frac{V^2}{P} = \frac{(10\text{ V})^2}{-100\text{ mW}} = -1000\Omega$$

B. Which direction is the current i_x flowing? From negative to positive.

C. Is this element producing or consuming power? It is producing power.

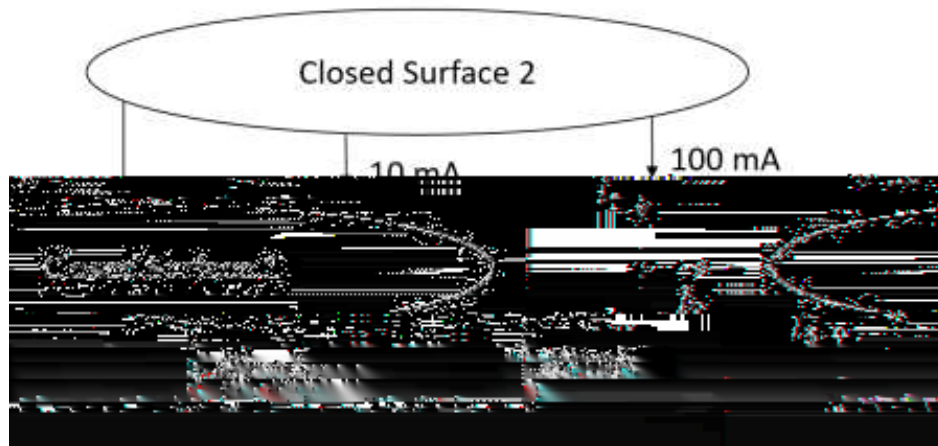Question 2: KCL states current entering a node is equal to current leaving a node. There is, however, no reason to restrict ourselves to simply nodes. It may be restated as currents entering a closed surface have to equal currents leaving a closed surface. That being said, solve for the currents (I_1, I_2, I_3).



$$\begin{aligned}\text{Closed Surface 1} &= -40mA + 30mA + 100mA + 10mA - I_2 \\ &= 0.1A - I_2\end{aligned}$$

$$I_2 = 0.1A$$

$$\text{Closed Surface 2} = -10mA - 100mA - I_1$$

$$I_1 = -0.11A$$

$$I_1 + I_2 + I_3 = 0$$


$$I_3 = -I_1 - I_2$$

$$I_3 = 0.11A - 0.1A$$

$$I_3 = 0.01A$$


$$(I_1; I_2; I_3) = (-0.11A; 0.1A; 0.01A)$$

Question 3:

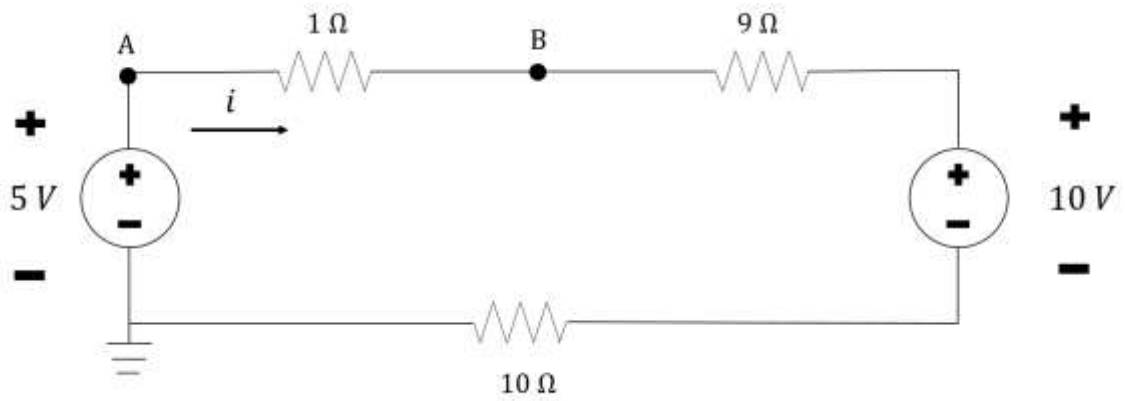

- A. Find the current i .
- B. Find V_{AB} , the voltage across the 1Ω resistor.
- C. Is the voltage at node B higher or lower than the voltage at node A?

Question 4:

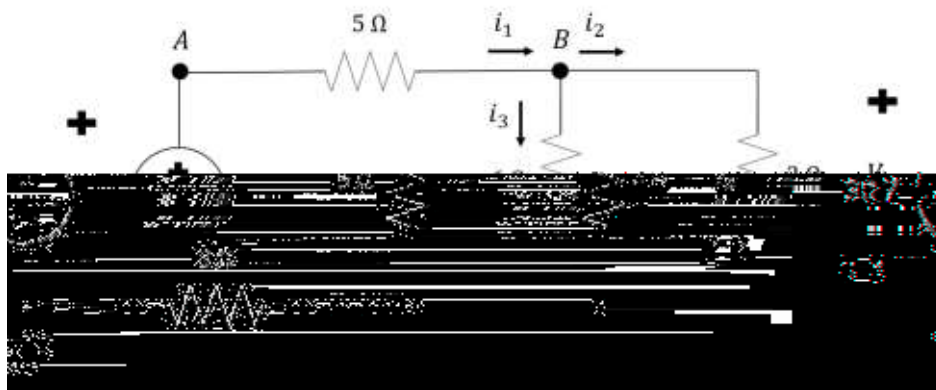

- A. Solve for the current (i_1 , i_2 , i_3) as well as V_x .
- B. What is the voltage across the 5Ω resistor (V_{AB})?