

Design & Simulate 18

ECE2204 CRN:82929

Jacob Abel

October 17, 2018


Problem 18.3-10.a.1:

Design

Determine the modes of the transistors, determine the MOSFETs responsible for each border point, and calculate V_{in} and V_O for each border point.

Additionally, determine the power of the circuit for the maximum and minimum V_{in} . Assume

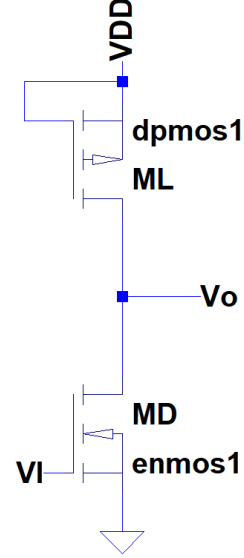$V_{TND} = 1V$, $V_{TPL} = 2V$, $K_{ND} = 50\mu A/V^2$, $K_{PL} = 10\mu A/V^2$, and $V_{DD} = 5V$.



$$V_O = V_{DD} - V_{TPL} = 5V - 2V = 3V$$

$$I_{SL} = K_{PL}V_{SD}^2 = K_{PL}V_{TPL}^2 = (10\mu A/V^2)(2V)^2 = 40\mu A$$

$$I_{SL} = K_{ND}(V_I - V_{TND})^2$$

$$V_I = \sqrt{\frac{I_{SL}}{K_{ND}}} + V_{TND} = \sqrt{\frac{40\mu A}{50\mu A/V^2}} + 1V = 1.895V$$

$$P_{Vmin} = V_I I_{SL} = (1.895V)(40\mu A) = 75.8\mu W$$

$$I_{SL} = K_{PL}(V_{SGL} + V_{TPL})^2 = K_{PL}(V_{TPL})^2 = (10\mu A/V^2)(2V)^2 = 40\mu A$$

$$V_O = \sqrt{\frac{I_{SL}}{K_D}} = \sqrt{\frac{40\mu A}{50\mu A/V^2}} = 0.9V$$


$$V_I = V_O + V_{TND} = 0.9V + 1V = 1.9V$$

$$P_{Vmax} = V_I I_{SL} = (1.9V)(40\mu A) = 76\mu W$$


Initially, the circuit is in region 1 and therefore ML is in the Ohmic Mode and MD is off. Between $V_I = 1.895$ and $V_I = 1.9V$ the circuit is in region 2 and both transistors switch to Saturation Mode. Past $V_I = 1.9V$, the circuit enters region 3 and ML transitions back into Ohmic Mode.

At the first transition $V_O = 3V$ and $P_{Vmax} = 76\mu W$. At the second transition $V_O = 0.9V$ and $P_{Vmin} = 75.8\mu W$.

Validation

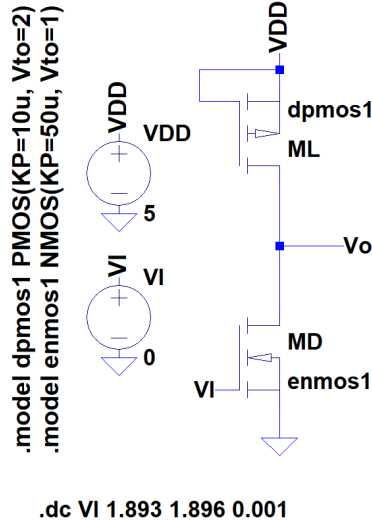

LTSpice Implementation

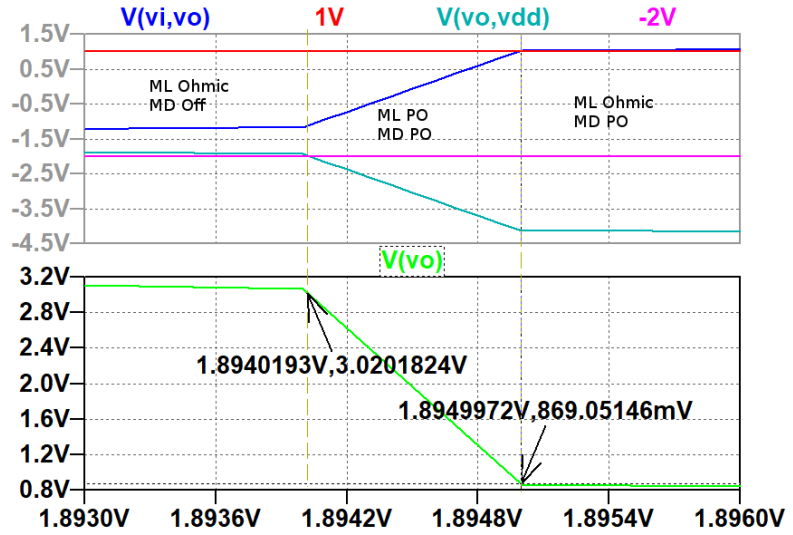

$$Err_{V_{I1}} = \frac{|1.895 - 1.894|}{1.895} = 0.05\%$$

$$Err_{V_{I2}} = \frac{|1.9 - 1.895|}{1.9} = 0.26\%$$

$$Err_{V_{O1}} = \frac{|3 - 3.02|}{3} = 0.60\%$$

$$Err_{V_{O2}} = \frac{|0.9 - 0.869|}{0.9} = 3.4\%$$

Deviation on V_{O2} is due to marker placement error.

This assignment should demonstrate a basic ability to manipulate, design, and analyse depletion load MOSFET circuits.

I have neither given nor received unauthorized assistance on this assignment.